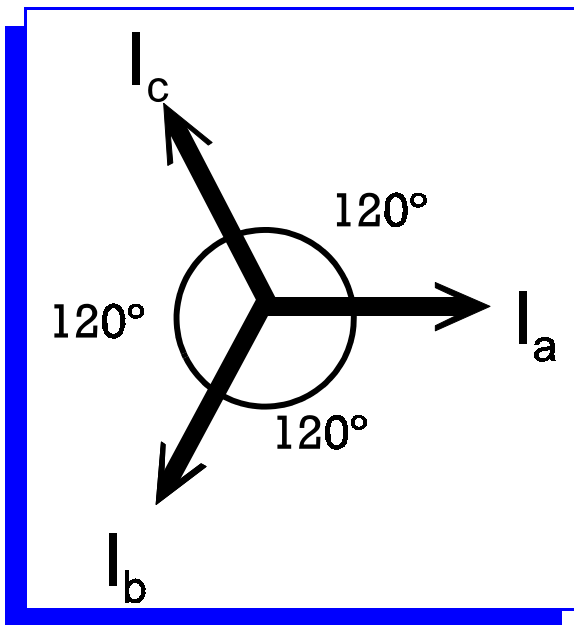


## Introduction

The method of symmetrical components is a mathematical technique that allows the engineer to solve unbalanced systems using balanced techniques.

Developed by C. Fortescue and presented in an AIEE paper in 1917, the method allows the development of sets of balanced phasors, which can then be combined to solve the original system of unbalanced phasors.




**Figure 1** – Balanced 3 Phase System

Figure 1 illustrates a balanced, three-phase system of phasors. Note that each of the three phasors are equal in magnitude and displaced by 120 degrees from the others. Further, the direction of positive rotation is counterclockwise. Such a diagram might represent the three phase currents in a normally operating power system.

Figure 2, on the other hand, shows an unbalanced system, where the three phasor magnitudes are not equal,

$$|I_a| \neq |I_b| \neq |I_c|$$

and the three phase angles are not necessarily 120 degrees. The phasors labeled as the *Original System* in Figure 2 are typical of the currents in a three phase system with a short circuit to ground on phase A.

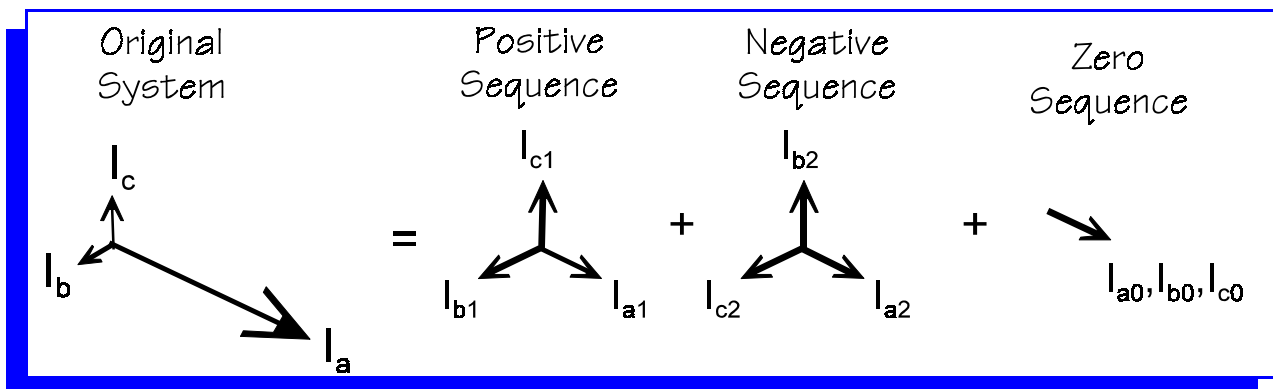

**Figure 2** – Unbalanced 3 Phase System

The concepts illustrated in Figure 2 are stated mathematically in Equations (1), (2), and (3).

$$(1) \quad I_a = I_{a0} + I_{a1} + I_{a2} \quad (2) \quad I_b = I_{b0} + I_{b1} + I_{b2} \quad (3) \quad I_c = I_{c0} + I_{c1} + I_{c2}$$

If the vector operator 'a' is defined as:

$$(4) \quad a = 1 \angle 120^\circ$$

then:

$$(5) \quad I_{b1} = a^2 I_{a1} \text{ and } I_{b2} = a I_{a2} \quad (6) \quad I_{c1} = a I_{a1} \text{ and } I_{c2} = a^2 I_{a2}$$

∴

$$(7) \quad I_a = I_{a0} + I_{a1} + I_{a2} \quad (8) \quad I_b = I_{a0} + a^2 I_{a1} + a I_{a2} \quad (9) \quad I_c = I_{a0} + a I_{a1} + a^2 I_{a2}$$

## The Sequence Quantities

From Equations (7), (8), and (9) you can see that each phase wire will have its own, independent sequence currents flowing in it. The A phase wire, for example, will have its own positive sequence current ( $I_{a1}$ ), negative sequence current ( $I_{a2}$ ), and zero sequence current ( $I_{a0}$ ). The total current in any phase wire is then expressed as the sum of the three sequence components.

It is especially important to note that, even though the total current in any given phase may be equal to zero, the individual sequences are not necessarily equal to zero. In a single phase fault, for example,  $I_b$  and  $I_c$  are both zero; however, the phase B and phase C sequence components ( $I_{b1}, I_{b2}, I_{b0}, I_{c1}, I_{c2}, I_{c0}$ ) are not zero.

Equations (7), (8), and (9) can be solved for the sequence components as shown in Equations (10), (11), and (12). You can see that for any given set of phasors ( $I_a, I_b, I_c$ ), there exist three unique sequence phasors ( $I_{a0}, I_{a1}, I_{a2}$ ). Equations (13), (14), and (15) show the same solution applied to the power system voltages.


$$(10) \quad I_0 = \frac{1}{3}(I_a + I_b + I_c) \quad (11) \quad I_1 = \frac{1}{3}(I_a + a I_b + a^2 I_c) \quad (12) \quad I_2 = \frac{1}{3}(I_a + a^2 I_b + a I_c)$$

$$(13) \quad V_0 = \frac{1}{3}(V_a + V_b + V_c) \quad (14) \quad V_1 = \frac{1}{3}(V_a + a V_b + a^2 V_c) \quad (15) \quad V_2 = \frac{1}{3}(V_a + a^2 V_b + a V_c)$$

Notice also, that by convention, the phase subscript is dropped. Thus  $I_{a1}$  becomes  $I_1$ . This causes no confusion since the convention is generally applied throughout the industry.

### The Sequence Networks

1. For any three phase system, three sets of independent sequence components can be derived for both voltage and current.
2. Since the three sequence components are independent, we may infer that each sequence current flows in a unique network creating each sequence voltage.

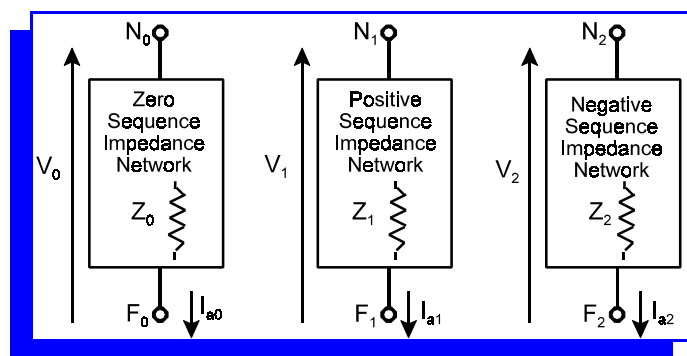


**Figure 3** – Sequence impedance networks

Taken together, these two points imply the existence of sequence impedance networks as shown in Figure 3. Each sequence network represents the entire power system reduced to a single impedance. The  $N_x$  terminals are the neutral or return terminals for each network. For a short circuit study, the  $F_x$  terminals represent the assumed point of the short circuit.

As soon as the engineer has developed the three sequence impedance networks, the analysis of the system may proceed.

### System Short Circuits

Four types of short circuits may occur in a power system. The basic configuration of each short circuit is shown in Figure 4. Note that the nature of each type of short circuit creates certain mathematical boundary conditions which are listed in Table 1. These boundary conditions are particularly useful since they can be used to determine how to model a faulted system with the sequence impedance networks.

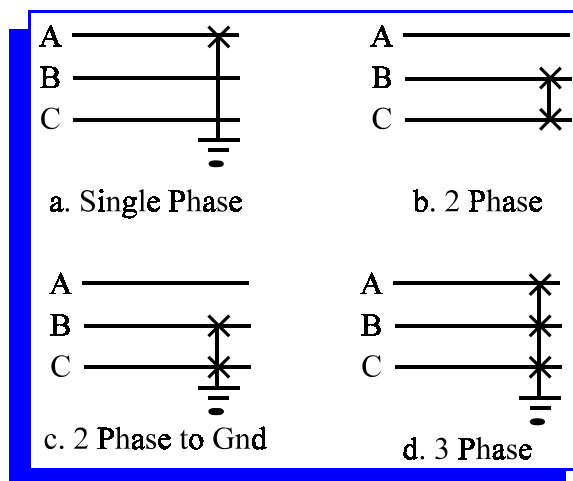

**Figure 4** – Four types of system faults

**Table 1** – Fault system boundary conditions

Type of fault	Boundary conditions
Single Phase	$I_b = I_c = 0$ and $V_a = 0$
2 Phase to ground	$I_a = 0$ and $V_b = V_c = 0$
2 Phase	$I_b = -I_c$ and $V_b = V_c$
3 Phase	$I_a + I_b + I_c = 0$ and $V_a = V_b = V_c$

### Modeling Short Circuits

The model for a single phase short circuit will be developed in this paper. The three other types of connections may be developed using similar methods. For a single phase short circuit, first we consider the current boundary conditions which state that  $I_b=I_c=0$ .

Inserting the boundary conditions into equations (10), (11), and (12) results in:


$$(16) \quad I_0 = \frac{1}{3}(I_a + 0 + 0) = \frac{1}{3}I_a \quad (17) \quad I_1 = \frac{1}{3}(I_a + 0 + 0) = \frac{1}{3}I_a \quad (18) \quad I_2 = \frac{1}{3}(I_a + 0 + 0) = \frac{1}{3}I_a$$

The voltage boundary condition is that  $V_a=0$ . Substituting this condition into equations (13), (14), and (15) and adding the three gives Equation (19).


$$(19) \quad V_0 + V_1 + V_2 = \frac{1}{3} \left[ (V_b + aV_b + a^2V_b) + (V_c + aV_c + a^2V_c) = 0 \right]$$

Equations (16), (17), (18), and (19) may be seen as statements of Kirchoff's laws — the sum of the voltage drops around a series circuit is equal to zero and the currents in a series circuit are equal throughout. Thus Figure 5 illustrates the proper connection for a single phase to ground fault.

By similar reasoning, Figures 6, 7, and 8 can be shown to be the correct circuits for two phase to ground, two phase, and three phase short circuits, respectively.

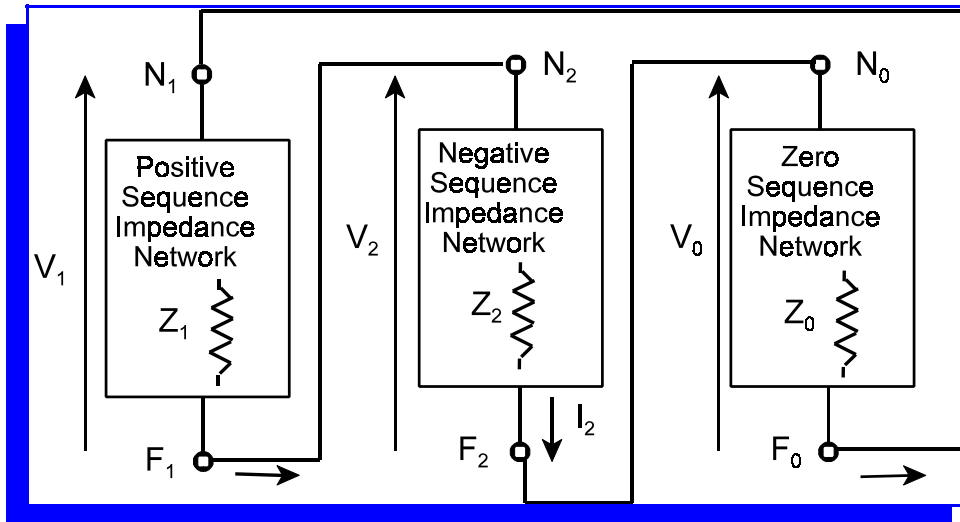


**Figure 5** – Sequence network connections, single phase to ground fault

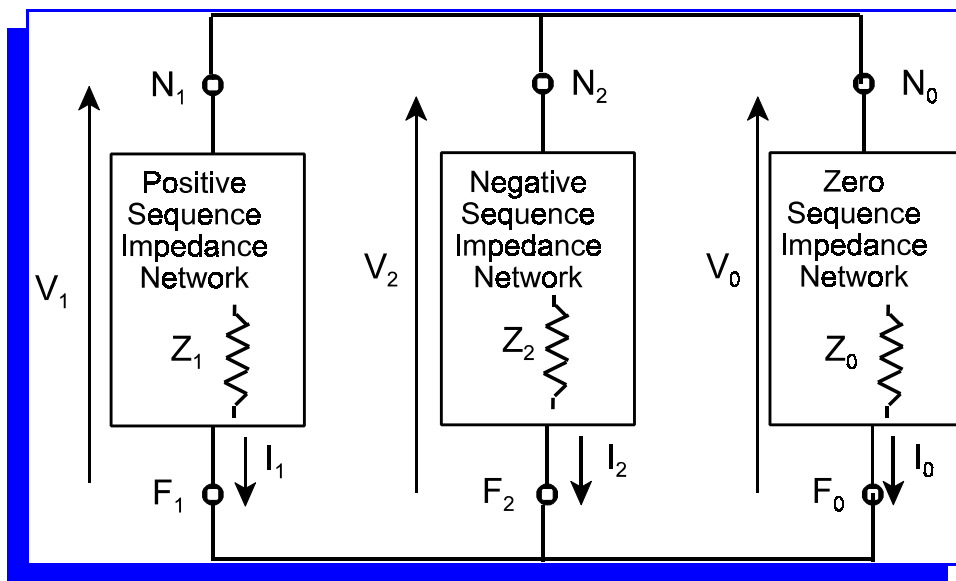


**Figure 6** – Sequence network connections, two phase to ground fault

# TECHNICAL BULLETIN — 006 Symmetrical Components Overview

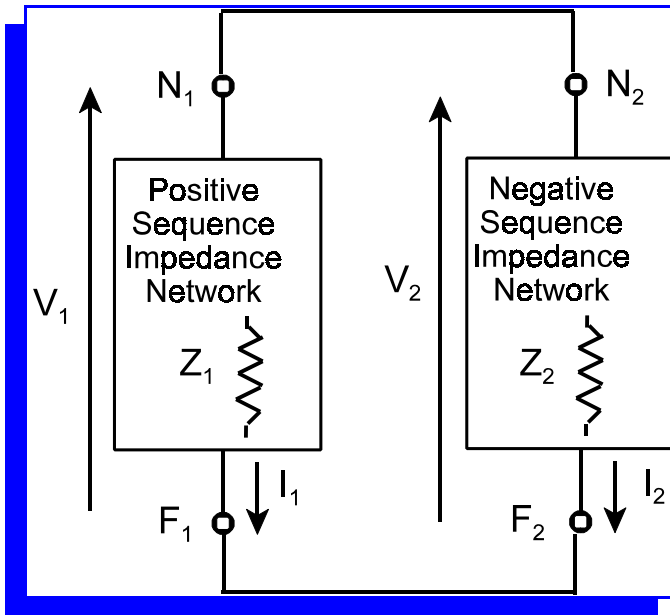

**Figure 7** – Sequence Network Connections, 2 phase fault

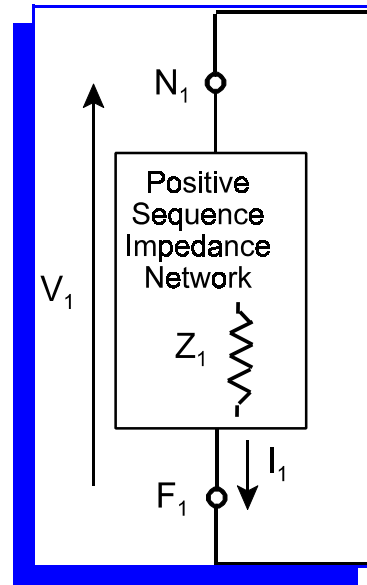

**Figure 8** – Sequence network connections, 3 phase fault